
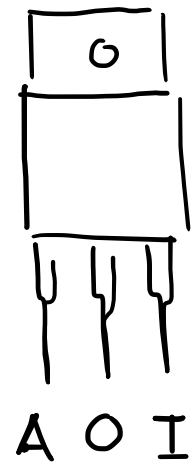


LM 317

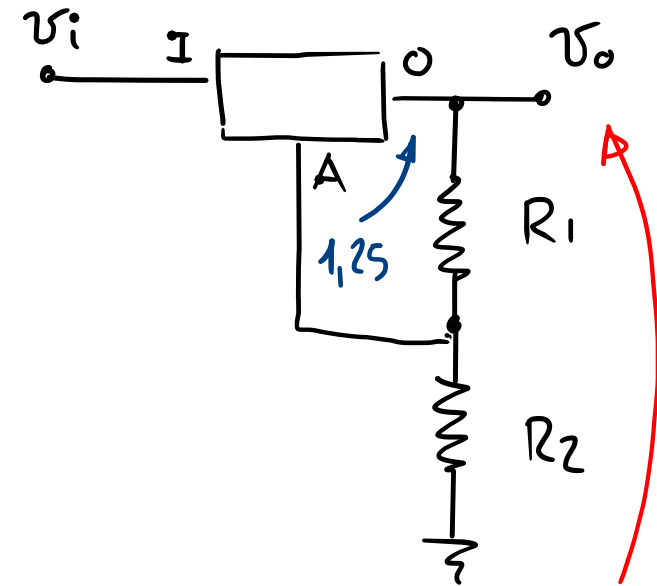

1,5A



$$V_o = 1,25 \left(1 + \frac{R_2}{R_1} \right)$$


$$R_1 = 1k \quad V_o \dots$$

$$R_2 \approx \dots$$


$$V_o = 4V$$

$$R_2 \approx 2,2k \Omega$$

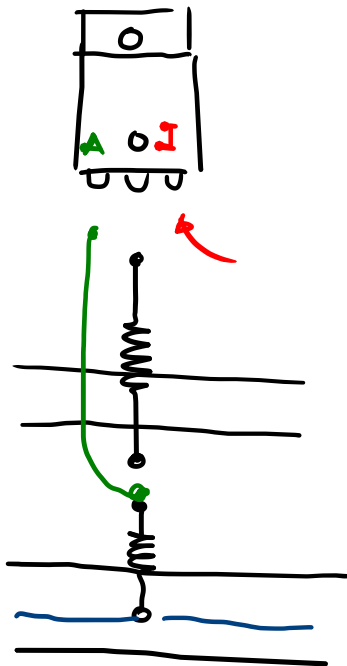
$$R_2 = \frac{V}{I} = \frac{V_o - 1,25}{\frac{1,25}{R_1}}$$



② LM 317 STAB. TENS. REGOLABILE

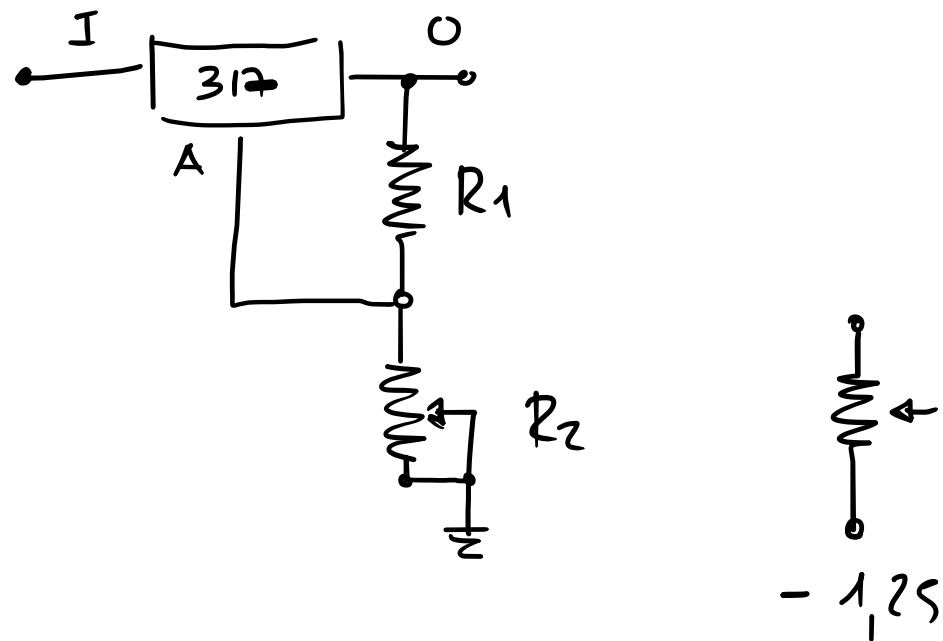

③ LM317 REG. I

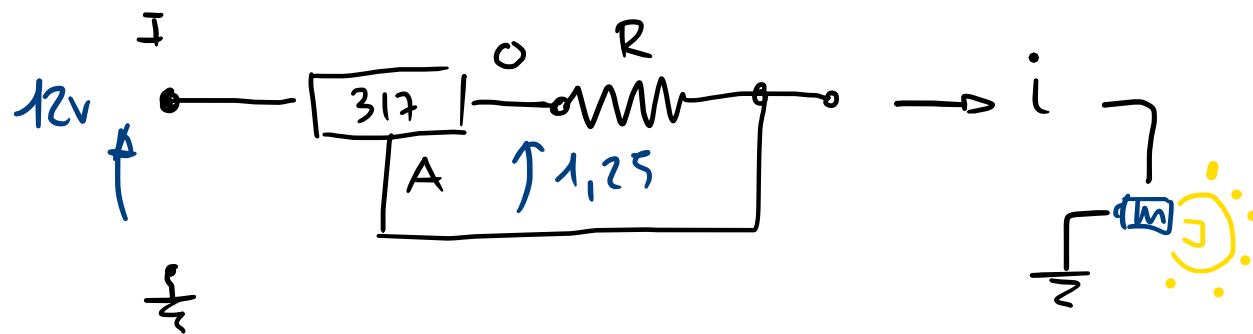

$$i = \frac{1,25V}{R}$$

$$R = \frac{1,25V}{i}$$

$$i = \frac{1,25}{1000} = 1,25 \text{ mA}$$

$$i = \frac{1,25}{100} = 12,5 \text{ mA}$$

$$i = \frac{1,25}{10} = 125 \text{ mA}$$

$$P = i^2 \cdot R = 0,125^2 \cdot 10 \approx 0,156 \text{ W}$$

