

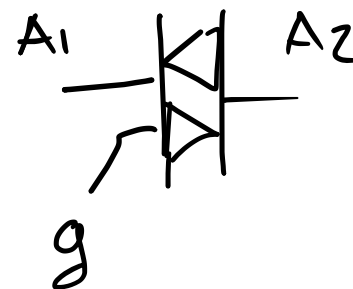
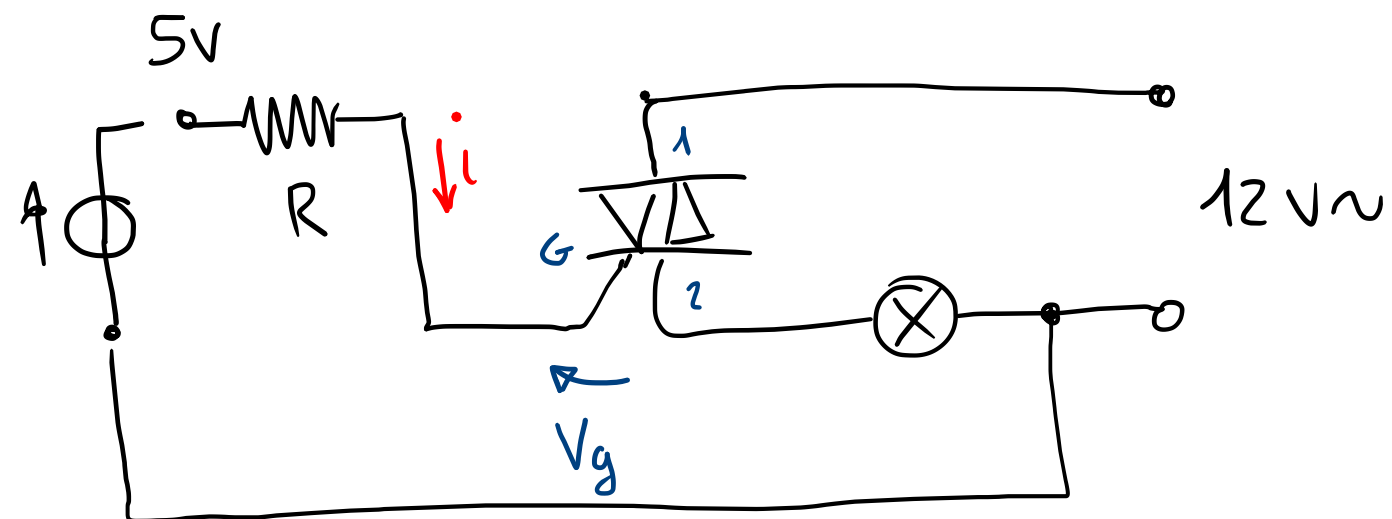
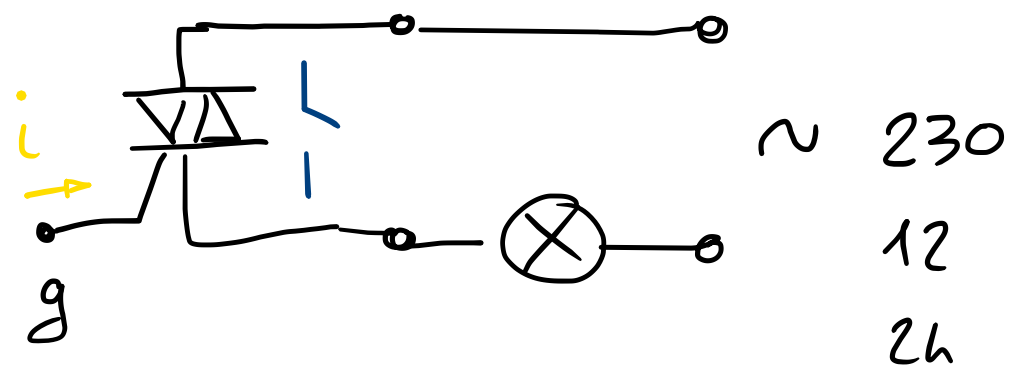


TRIAC



↳ TRIode per AC

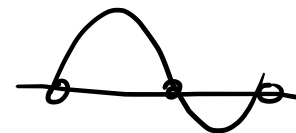

BTA08-600

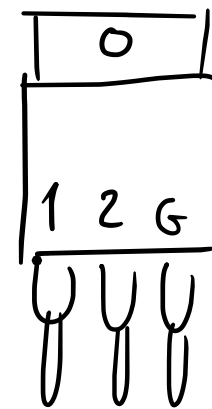
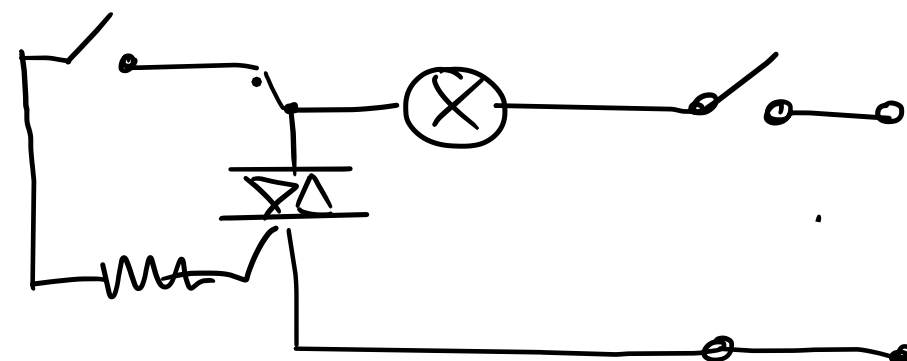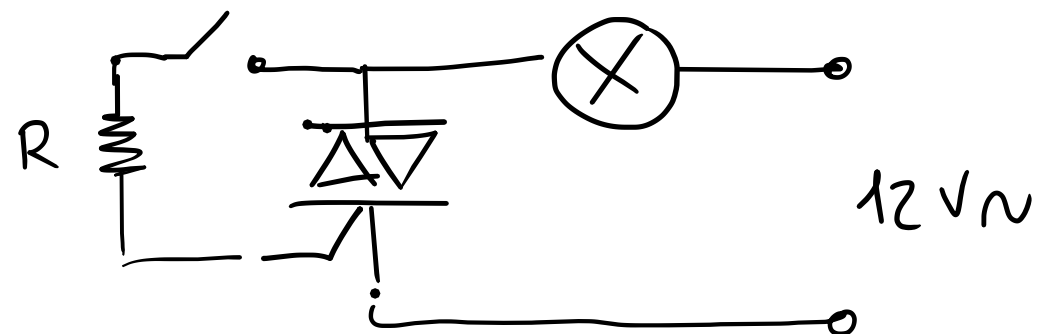
$$R = \frac{V}{I} = \frac{5 - V_G}{i_g} = \frac{5 - 1,3}{50\mu A} \approx 74 \Omega$$



$$R = \frac{12 - 2}{50\text{mA}} = \frac{10}{50\text{mA}} = 0.2 \approx 200\Omega$$